

PAN AFRICA CHRISTIAN UNIVERSITY

DIPLOMA INFORMATION COMMUNICATION TECHNOLOGY

END OF TERM EXAMINATION

DEPARTMENT: COMPUTING & INFORMATION TECHNOLOGY

COURSE CODE: DICT0122

CAMPUS: ROYSAMBU

COURSE TITLE: COMPUTER ELECTRONICS

EXAM DATE: 7th April 2025


TIME: 2:00 PM

INSTRUCTIONS


- This exam carry a total of SIX Questions of [10 Marks Each]
- Section One (I) is compulsory.
- Answer any 3 (Three) Questions from Section Two (II)
- Read all questions carefully before attempting.

SECTION ONE: (COMPULSORY)**10 MARKS****QUESTION ONE**

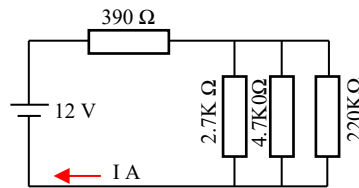- Explain the working principle of a N-P-N transistor. [3 Marks]
- Given the circuit below, calculate the current flowing through the circuit. [2 Marks]



- Convert the following numbers into their binary equivalent. [2 Marks]
 - 12_8
 - 10_{16}
- Using a Truth Table, explain how the following logic circuit works. [3 Marks]

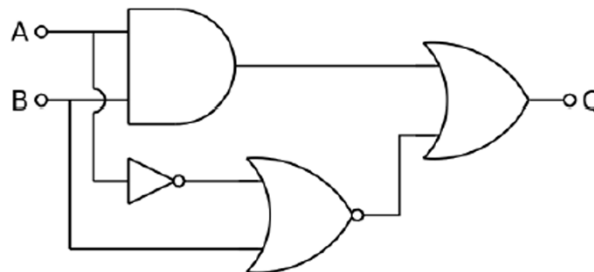**SECTION TWO: (ANSWER ANY THREE (3) QUESTIONS)****30 MARKS****QUESTION TWO.**

- Distinguish between computer memory and computer storage. [2 Marks]
- Discuss three characteristics of computer memory. [3 Marks]
- Distinguish between Cache and Primary (Main) Memory. [2 Marks]
- Discuss two types of Magnetic Disks and explain why Solid-State disk is preferred over magnetic disks. [3 Marks]

QUESTION THREE.

- There are two main ways that resistors are used in electronics. Name and explain the two ways. [4 Marks]
- Design a circuit with both series and parallel configurations. [4 Marks]
- Discuss how transformers are used in electronic devices. [2 Marks]

QUESTION FOUR.

Given the Truth Table below.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Write the Boolean expression of the above table. [2 Marks]
- Minimize the expression using the Boolean Algebraic Laws. [3 Marks]
- Design a circuit using AND, OR, and NOT gates to implement the Boolean expression $F(ABC)=A'B+AB'C$. [5 Marks]

QUESTION FIVE.

- Design a D flip-flop circuit and explain its operation. [3 Marks]
- Use the above flip-flop to build a 2-bit binary counter. [5 Marks]
- Discuss two advantages of using JK flip-flop in sequential circuits. [2 Marks]

QUESTION SIX.

- Investigate how 5G technology can be used in the transportation industry. [3 Marks]
- Discuss the role of electronics in addressing challenges related to the integration of renewable energy into existing power grids. [3 Marks]
- Differentiate between "half-wave" and "full-wave rectifiers". [4 Marks]

-END-